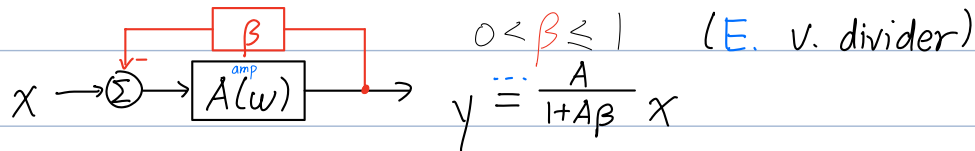



Feedback



$0 < \beta \leq 1$ (E. v. divider)

E. $G=2 \rightarrow \beta = \frac{1}{2}$, $y \approx 2x$, indep. of $A \gg 1$


E. distortion

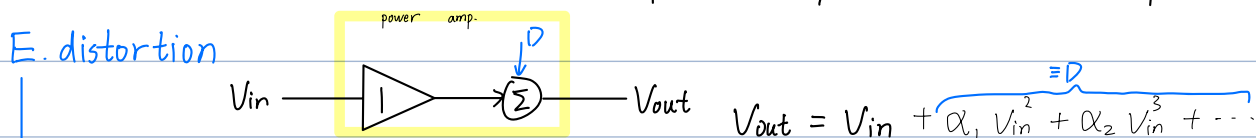

$$V_{out} = D + A(V_{in} - V_{out})$$

$$V_{out} = \frac{D}{1+A} + \frac{A}{1+A} V_{in} \approx V_{in} \text{ if } A \gg 1$$

Diodes

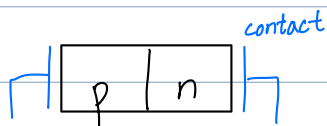

M-S potential fixed


p-n potential depends on V_{ext}

eg. $i_d = I_s (e^{V_d/n\phi_t} - 1)$

saturation, $\sim 10^{-14}$
 $V_d/n\phi_t \sim 26mV$
 $1 \leq n \leq 2$

$$\phi_t = \frac{kT}{|q|}$$

E.

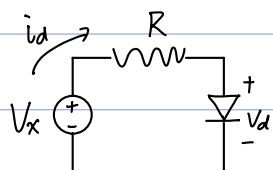


$$\frac{V_x - V_d}{R} = i_d = I_s e^{V_d/n\phi_t}$$

transcendental : (

① $V_x \sim 100V \rightarrow V_d \approx 0$ in FB


$\rightarrow$ ideal diode

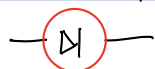

② $V_x \sim 10V \rightarrow$ drop 0.6V, 0.3, 1.5

$\rightarrow$ fixed-drop model

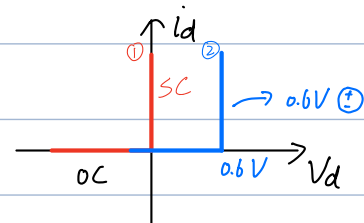③ $V_x \sim 1V \rightarrow$ full Shockley



a. numerical

$$\frac{V_x - V_d}{R} = I_s e^{V_d/n\phi_t}$$

E. $R=100$, $V_x=1$

(1) guess $V_d = 0.5V$

(2) $i_d = \frac{1-0.5}{100} = 5mA$

(4) $i_d = 3mA$

(3) $V_d = 0.7V$


(5) $V_d = 0.687V$

b. graphical Load line analysis

E. $R=1k$, $V_x=1$

load line: $\frac{1-V_d}{1k} = i_d$

find intersection w/ Shockley

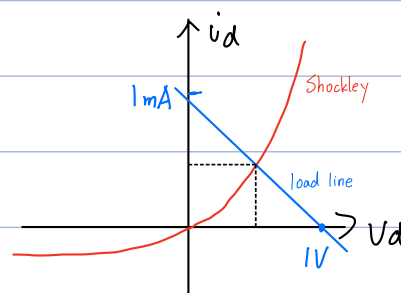

Non-lin apps

1. log ①

$$V_{d1} = n\phi_t \ln\left(\frac{i_{d1}}{I_s} + 1\right) \quad \text{FB}$$


②

$$V_{d1} + V_{d2} = n\phi_t \ln \frac{i_{d1} i_{d2}}{I_s^2}$$

③

$$i_{out} = I_s e^{\frac{V_{d1} + V_{d2}}{n\phi_t}} = \frac{i_{d1} i_{d2}}{I_s} \rightarrow \text{analog } \otimes$$

V_d	$\sim i_d$
0.5	2.25μ
1	505
10	10^{153}

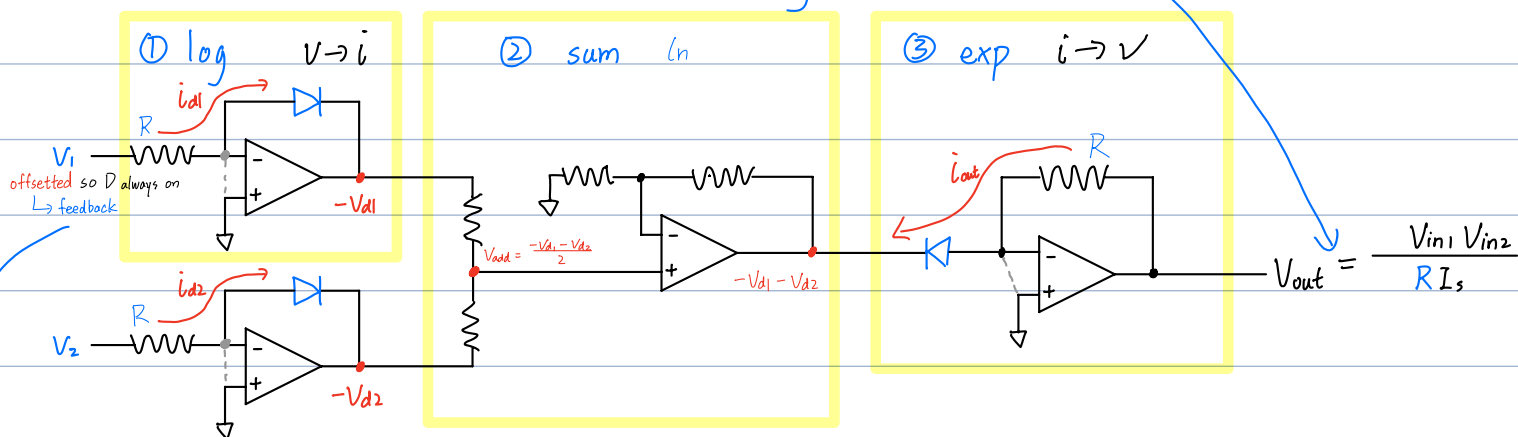


Input: offsetted sin waves. E. $V_1: 9k, V_2: 10k \Rightarrow V_{out}: 1k, 9k, 10k, 19k$

Feedback check 1. Shut down source

2. Remove opamp, connect V_{out} to V_{test}

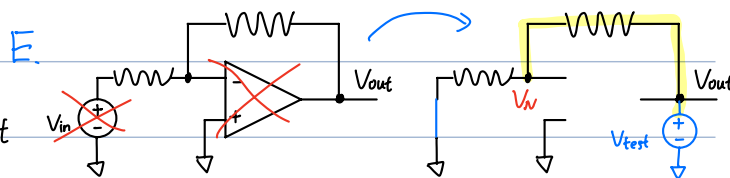3. See if any of V_{test} appears at V_{in}



2. Temp


$$V_d = n\phi_t \ln \frac{i_d}{I_s}$$

$$V_d = V_{d0} - 2 \text{ mV/K } (T - T_0)$$

Bandgap ref. $T \uparrow \rightarrow V_d \downarrow$, but $\Delta V_d \uparrow$, so we can weigh them and cancel $V_d \downarrow$ as $T \uparrow$

$$V_d = n\phi_t \ln \frac{I}{I_s}$$
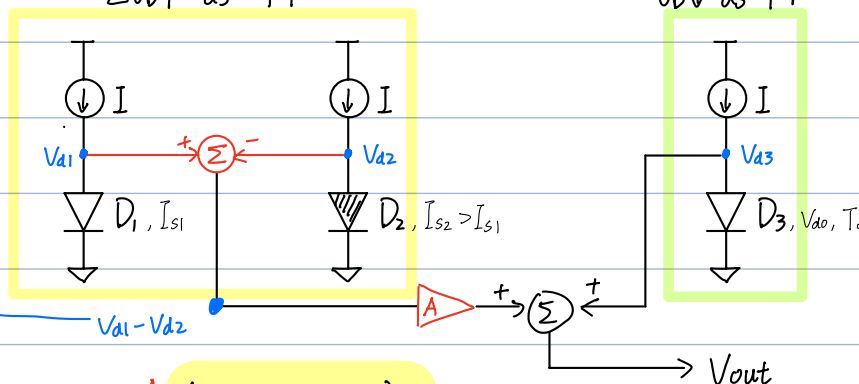
$$V_{d1} - V_{d2} = n \frac{kT}{q} \ln \frac{I_{s2}}{I_{s1}}$$



$$V_{out} = V_{d3} + A (V_{d1} - V_{d2})$$

$$= V_{d0} - 2 \text{ mV/K } (T - T_0) + A n \frac{kT}{q} \ln \frac{I_{s2}}{I_{s1}}$$

$$= V_{d0} + 2 \text{ mV/K } T_0 + T \left(-2 \text{ mV/K } + \frac{A n k}{q} \ln \frac{I_{s2}}{I_{s1}} \right)$$

$\rightarrow$ Choose A so V_{out} indep. of T

Kujik bandgap $\ominus$ feed., since $\ominus$ fed, $\oplus$ clipped only by D_1 .

$$V_p = V_N \rightarrow i_1 = i_2 \text{ if } R_1 = R_2$$

$$V_{out} = i_2 R_2 + V_{d1} = \frac{R_2}{R_3} (V_{d1} - V_{d2}) + V_{d1}$$

$$= \frac{R_2}{R_3} \left(\frac{nkT}{|q|} \ln \frac{i_1 I_{s2}}{i_2 I_{s1}} \right) + V_0 - 2mV_K (T - T_0)$$


$$= T \left[\frac{R_2}{R_3} \left(\frac{nk}{|q|} \ln \frac{I_{s2}}{I_{s1}} \right) - 2 \frac{mV}{K} \right] + [V_0 + 2 \frac{mV}{K} T_0]$$

Choose $\frac{R_2}{R_3}$ s.t. cancel

$n = 1.752$ for 1N4148

$$i_1 = \frac{V_{out} - V_{d1}}{R_1} = 5 \text{ mA} \rightarrow R_1 = R_2 = 250 \Omega \rightarrow R_3 = 26.2 \Omega$$

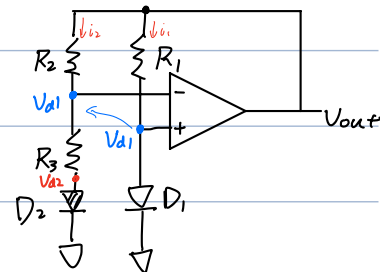Find slope of V_{d1} vs. $T \rightarrow$ recalculate $R_3 = 30.1 \Omega$



3. One-way $\rightarrow$ Peak detector

- Transformer $I_m = \frac{V_1}{j\omega L_1} \rightarrow$ want $\omega \uparrow$ ($L \rightarrow \infty$ for ideal)

- Half wave charge $\rightarrow$ stay at peak, not rms

+ I_{Load} (E. battery charger)

$V \downarrow$ linear


$$\Delta Q = \int_{T_{dis}} I_L dt$$

$$= T_{dis} I_L = C \Delta V \rightarrow \equiv V_R \text{ ripple}$$


$$C = \frac{T_{dis} I_L}{V_R}$$

if V_R small, $T_{dis} \approx T_p$, and for R load, discharge $\sim \exp$, $I_L \approx \frac{V_p}{R_L}$

Full-wave

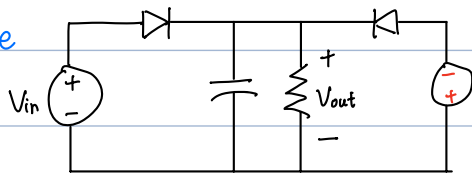


=

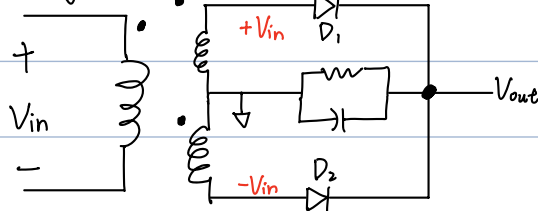

C only need hold half as long $C = \frac{I_L T_p / 2}{V_r}$

Can't breakdown $< 2V_{imp}$

Bridge

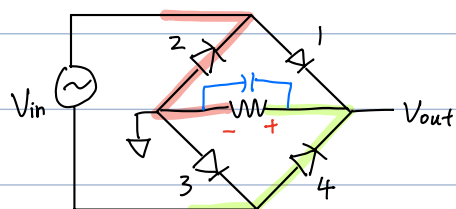

$V_{in} > 0 \rightarrow D_{1,3} \text{ on}$

$V_{in} < 0 \rightarrow D_{2,4} \text{ on}$

$< |V_{imp}|$


I_D 1. avg. = avg I_{load} (half) / $\frac{1}{2}$ avg I_{load} (full)

Long-term heating

2. peak $i_{peak} = C \frac{dV}{dt} + I_{load}$
 $\approx I_{load} (1 + 2\pi \sqrt{\frac{V_p}{2V_r}})$

Precision rect.

aka super diode

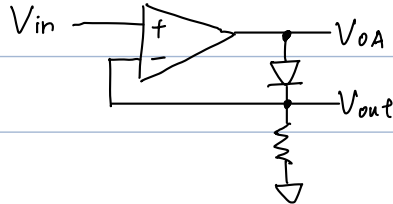

$V_{in} > 0$, no drop, $V_{out} = V_{in} = V_{OA} - V_D$


$V_{in} < 0 \rightarrow$ pulled down to 0 $V_{OA} = V_{SS}$

(inductive)
DC motor driver

$V = L \frac{di}{dt}$

Switch off $\rightarrow V = L \frac{di}{dt}$

$\rightarrow$ H-bridge

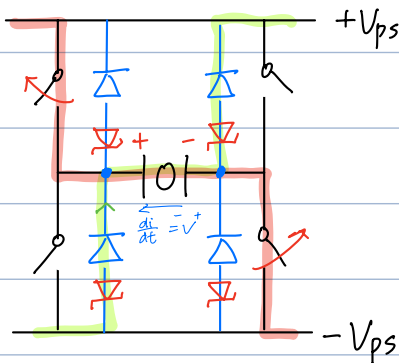


Need to time: $V = -2V_{ps} - 2V_D - 2V_Z$

D required to block fwd current

Z for more drop.

Zener


Power supply

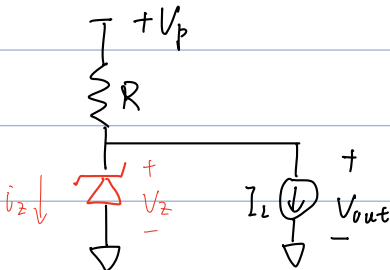

$V_{out} = V_Z$


$I_L = \frac{V_p - V_Z}{R} - i_Z$, wasteful

Regulator
(from peak detector)

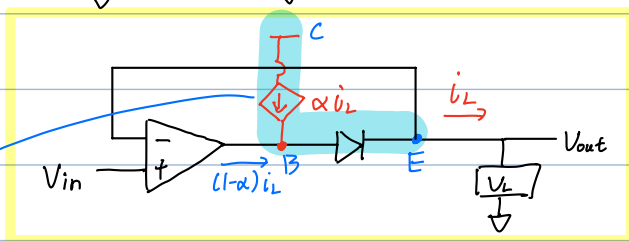


CCCS for more i_L drive


BJT

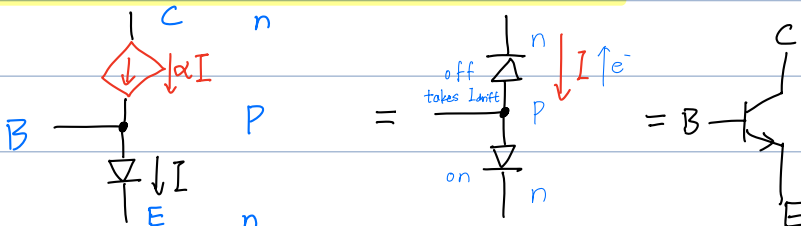

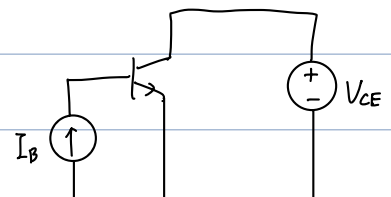$\alpha \equiv \frac{I_C}{I_E}$
 $\beta \equiv \frac{I_C}{I_B} = \frac{\alpha}{1-\alpha}$




E. Inverting

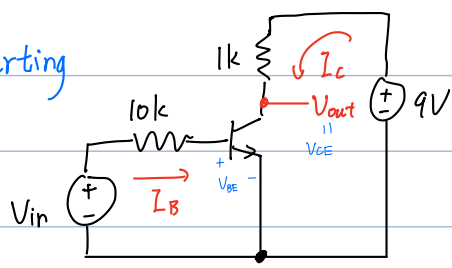

$$I_c = \frac{9V - V_{CE}}{1k}, \text{ inverting} \Rightarrow G_{\text{solve}}$$

$$I_c = f(V_{BE}, V_{CE})$$

Want to stay in active (E. bias)

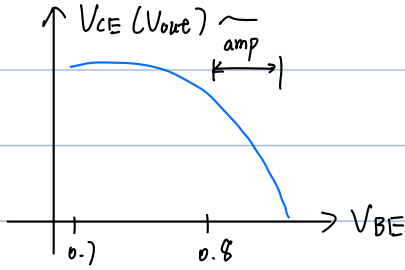

$$I_B = \frac{V_{in} - V_{BE}}{10k} = \frac{I_c}{\beta_{100}}$$

$$V_{in} = 100 I_c + V_{BE}$$

or plot V_{in} vs $V_{out} \rightarrow$ find slope


$I_B \xrightarrow{\text{lin}} I_c$ $V_{BE} \xrightarrow{\text{exp}} I_c$, better play w/ I_B

Approx. $V_{BE} = 0.75V$ (diode fixed drop)

$\rightarrow$ linear circuit

$$V_{out} = V_{CC} - i_c R_2 = V_{CC} - \left(\beta \frac{V_{in} - 0.75}{R_1} \right) R_2$$
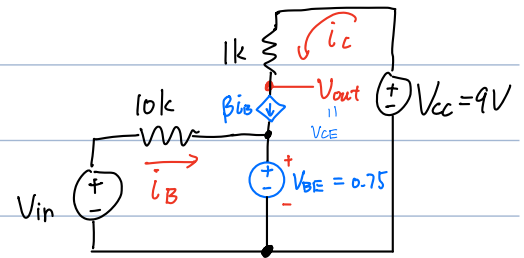
$$= V_{CC} - \frac{R_2}{R_1} \beta (V_{in} - 0.75)$$



Now let $V_{in} = V_{DC} + \Delta V$

$$V_{out} = \underbrace{V_{CC} - \frac{R_2}{R_1} \beta (V_{DC} - 0.75)}_{V_{bias}} - \underbrace{\frac{R_2}{R_1} \beta \Delta V}_{V_{out}} = -10 \Delta V$$

Small-sig $I_{Q, \text{quiescent}} = I_S e^{V_Q / \phi_t}$

$$V_D = V_Q + \Delta V \rightarrow i_D = I_Q e^{\Delta V / \phi_t}$$

$$= I_Q \left(1 + \frac{\Delta V}{\phi_t} \right) \rightarrow \text{lin!}$$

$$\Delta i = \frac{I_Q}{\phi_t} \Delta V \equiv \frac{\Delta V}{r_e} \rightarrow \text{small-sig emitter } R \equiv \frac{\phi_t}{I_Q}$$

E. 1. Find bias point (nonlin) with V_{in} (DC)




sim V_{out} , I_D

2. Turn off V_{in} , replace D w/ r_d

$$V_{out} = V_{in} \left(\frac{R}{r_d + R} \right)$$

3. Add $\Rightarrow V_{out} + V_{out}$

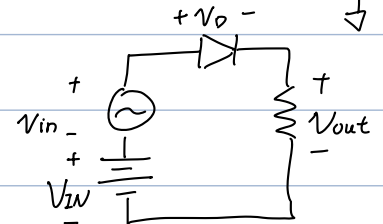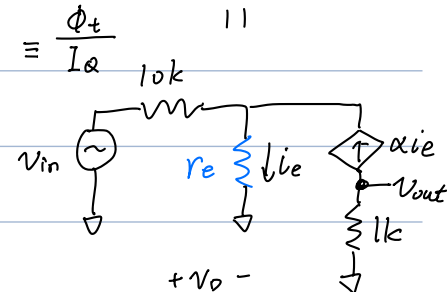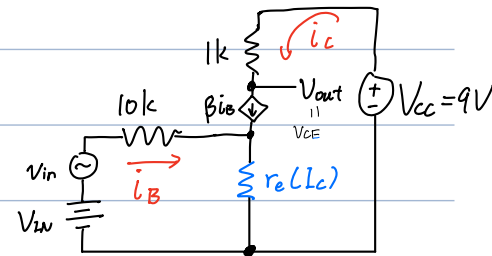E. bias point $\xrightarrow{\text{sim}} I_E \rightarrow r_e$




Bias point $V_{CE} = 9 - 1k I_C \stackrel{let}{=} 6V$

$$I_C = \beta \frac{V_{ZV} - 0.7}{100k} \approx 3m$$


SS

$$V_{out} = (-\alpha i_e) \cdot 1k$$


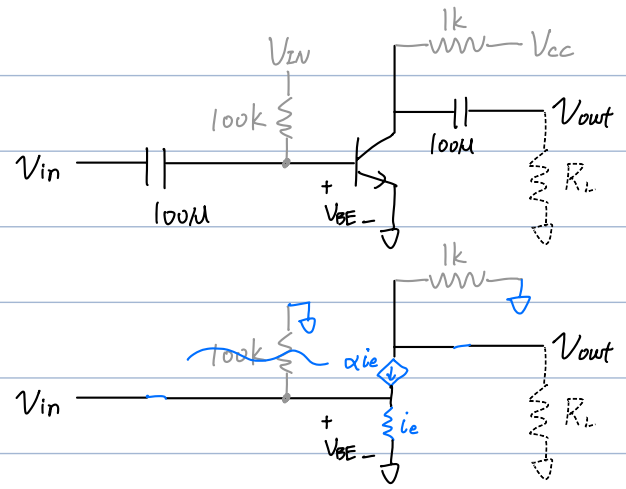
$$= (-\alpha \frac{V_{in}}{r_e}) \cdot 1k$$




SS NPN

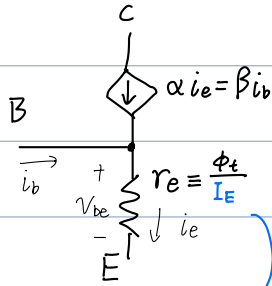

Hybrid π

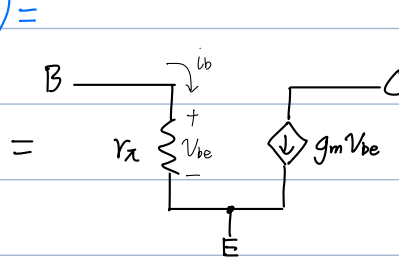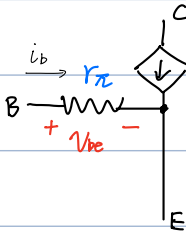

PNP

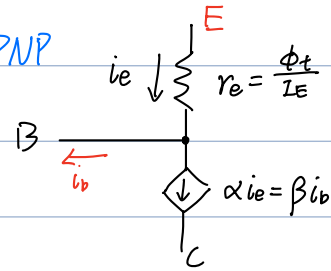

$$\alpha i_e = i_c = g_m V_{be}$$

$$g_m = \frac{\alpha}{r_e} = \frac{\alpha}{\phi_t / I_E} = \frac{I_C}{\phi_t}$$

$$i_e - i_c = i_b = \frac{V_{be}}{r_\pi}$$



$$r_\pi = r_e \frac{i_e}{i_b} = r_e (1 + \beta) = \frac{\beta}{g_m}$$

MOS Sym. device

$V_{GS} = 0$ Cutoff

$0 < V_{GS} < V_T$ Subthreshold

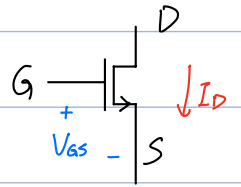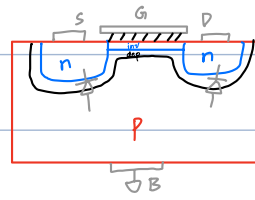$V_{GS} > V_T$ Lin. small $v_{DS} \rightarrow R$ controlled by V_{GS}



$v_{DS} \uparrow$
 $g \propto V_{GS} - V_T$

Triode channel pinched, $R \uparrow$, bad

Sat. $v_{DS} \geq V_{GS} - V_T$, all pinched, but $E \uparrow$, e^- drift thru
 $\rightarrow V_{CCS}$

Sat. $i_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \frac{v_{DS}}{V_A})$ for nonflat sat.

Lin. $i_D = \frac{v_{DS}}{R}$ where $R = \frac{1}{k' \frac{W}{L} (V_{GS} - V_T)}$

Amplifier Need V_{BIAS} for sat.

$$i_D = \frac{1}{2} k' \frac{W}{L} (V_{BIAS} - V_T)^2 + k' \frac{W}{L} (V_{BIAS} - V_T) \Delta V + \dots \Delta V^2$$

$\equiv I_{BIAS}$ region setup $\equiv g_m$, for amp.

$$= I_{BIAS} + g_m \Delta V$$

$$\rightarrow = \sqrt{2 k' \frac{W}{L} I_{BIAS}}$$

$$= \frac{1}{2} k' \frac{W}{L} V_{OD}^2 + g_m \Delta V$$

$$V_{OUT} = V_{DD} - \frac{1}{2} k' \frac{W}{L} V_{OD}^2 R_L$$

$$v_{out} = -g_m v_{in} R_L$$

$$\equiv V_{DD} - V_{DROP} \quad \equiv -A_v v_{in}$$


Design eq.

$$V_{OD} = \frac{2V_{DROP}}{|A_v|} \quad (A_v = g_m R_L = k' \frac{W}{L} V_{OD})$$

E. $V_T = 1V$, $k' \frac{W}{L} = 44.4 \text{ mA/V}^2$, $A_v = -20$, swing $= \pm 2V$, $V_{DD} = 10V$

$$\text{Let } V_{OUT} = 5V \rightarrow V_{DROP} = 5V \rightarrow V_{OD} = \frac{2V_{DROP}}{|A_v|} = 0.5V \xrightarrow{+V_T} V_{GS} = 1.5V$$

$$|A_v| = g_m R_L \rightarrow R_L = 900 \Omega$$

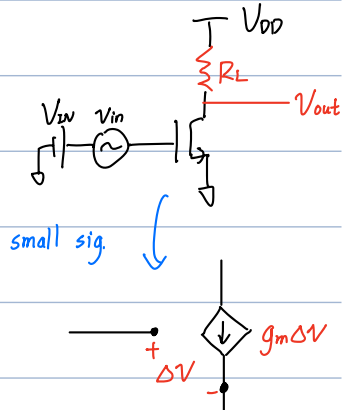


E. Find $\frac{W}{L}$, given $A_v = 20$, swing $\pm 2V$, $k' = 30 \text{ mA/V}^2$, $V_T = 0.3V$

Choose $R_L = 10k$, $V_{DROP} = 5V \rightarrow I_D = 500 \mu A$

$$|A_v| = g_m R_L = \sqrt{2 k' \frac{W}{L} I_D} R_L$$

$$\frac{W}{L} \approx 133.3$$

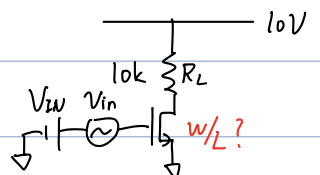

Safer to bias I_D , not V_{GS} (V_{DD}), due to $\sqrt{\quad}$


Bias I_{BIAS} pulls down V_s until V_{gs} is appropriate

indep. of V_T

E. $I_{BIAS} = R_s$ (variable) Given $V_T = 1V$, $k' \frac{W}{L} = 44.4 \frac{mA}{V^2}$, $V_{DD} = 10V$

want $A_v = -20$, swing = $\pm 2V$, $V_{DROD} = 5V$, $f_{min} = 20Hz$

$\rightarrow V_{OD} = \frac{2V_{DROD}}{|A_v|} = 0.5V$, $V_{gs} = V_{OD} + V_T = 1.5V$, $R_o = \frac{|A_v|}{g_m} = \frac{1}{k' \frac{W}{L} V_{OD}} = 900\Omega$, $I_D = \frac{1}{2} k' \frac{W}{L} V_{OD}^2 = 5.55mA$

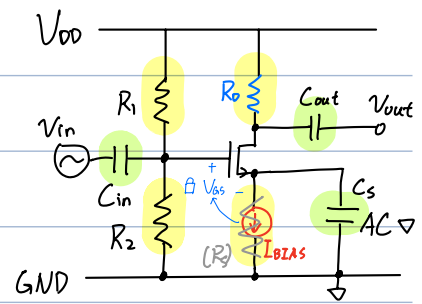

Swing $V_{D,min} = 3V$, need $V_{gs} \leq V_T$ for sat.

$$V_{gs} = V_{GD} + V_{DS}$$

$V_{OD} + V_T \geq V_T + V_{DS} \rightarrow V_{DS,min} = V_{OD} = 0.5V$

Bias Choose $V_s = 1V \rightarrow R_s = \frac{V_s}{I_D} = 180\Omega$

$V_{gs} \rightarrow V_{gs} = 2.5V \rightarrow$ make $R_1 = 75k$, $R_2 = 25k$

($10k \sim 100k$)

Filter HPF to block DC

C_{in} $f_{in} = \frac{1}{2\pi C_{in}(R_1 || R_2)} = \frac{f_{min}}{10} \rightarrow C_1 = 4.24 \mu F$

C_s $g_m(V_g - V_s) = i_D = V_s \frac{1 + sR_sC_s}{R_s}$ (classical approach)
 $V_s = V_g \frac{g_m R_s}{1 + g_m R_s + sR_sC_s}$

corner at $1 + g_m R_s = \omega R_s C_s$

$C_s = 2.2mF$ (R_s only 180Ω)

C_s will be much smaller if $R_s \uparrow$ ($\rightarrow \downarrow$)

if no C_s , feedback at both AC/DC ($V_{gs} \uparrow \rightarrow i_D \uparrow \rightarrow V_s \uparrow \rightarrow V_{gs} \downarrow \rightarrow \dots$)

$$V_{out} = -(g_m V_{gs}) R_D$$

$V_{gs} = V_{in} - g_m V_{gs} R_s = \frac{V_{in}}{1 + g_m R_s}$

$A_v = \frac{V_{out}}{V_{in}} = \frac{-g_m R_D}{1 + g_m R_s} \rightarrow$ neg. feedback, but improves distortion at same output swing
 $\approx -\frac{R_D}{R_s}$ if $g_m R_s \gg 1$



C_{out} depends on R_{in} of next stage

model simple FET NMOS (k_p , W , L , V_{to})


PMOS pull G down for I_D

$I_D > 0$ for $V_{sg} > |V_{Tp}|$ and $V_{sd} > 0$

$$I_D = \frac{1}{2} k_p' \frac{W}{L} (V_{sg} - |V_{Tp}|)^2$$

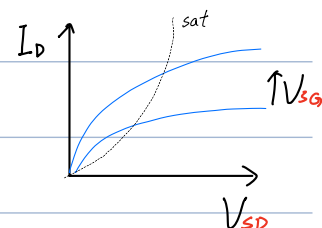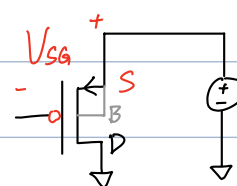

Load

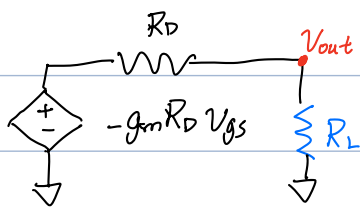


$$|A_v| = g_m R_D \frac{R_L}{R_L + R_D} = g_m (R_D \parallel R_L) \quad (\text{divided})$$



→ Buffer (follower) (HW)

$$I_D = \text{const.} \xrightarrow{\text{SS}} i_D = 0 \rightarrow V_{gs} = 0 \rightarrow V_{out} = V_{in}$$

SS.

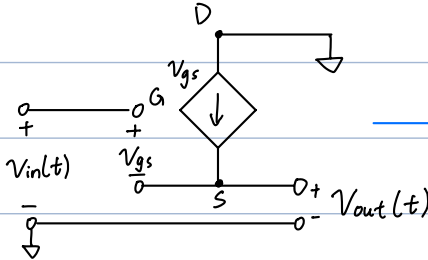

Th.

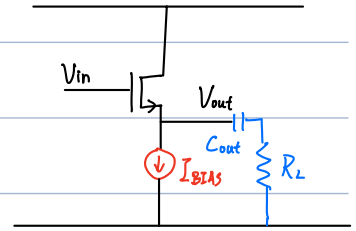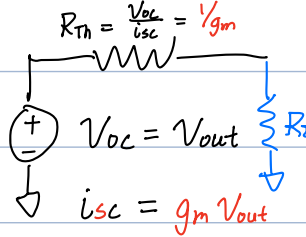

$$V_L = V_{in} \frac{R_L}{R_L + 1/g_m} \quad 1/g_m \sim 10 \Omega, \text{ small}$$



$$W_{\text{corner}} = \frac{1}{C_{out}(R_L + 1/g_m)}$$

Make sure I_D swing remains active ($I_{BIAS} \pm \frac{V_{out}}{R_L}$), else distorted

I_{BIAS} setup ($V_{SG} = V_{SD} \rightarrow I_D$)

R just to set V_{SG} for $k \times \text{PMOS} \rightarrow \text{mirror}$


PMOS implementation

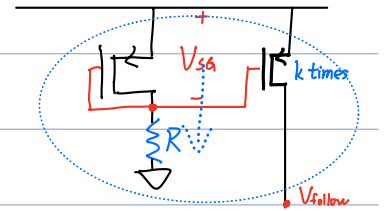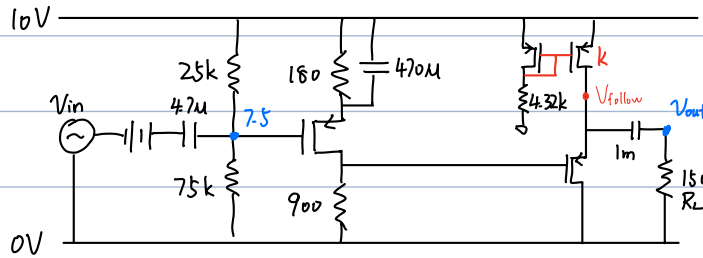

Current mirror I_{ref} to all analog cells


$$I_{ref} \xrightarrow{\text{pulls}} V_{sg} = V_{sg, \text{others}} \rightarrow I_{\text{others}}$$

Need to ensure sat.

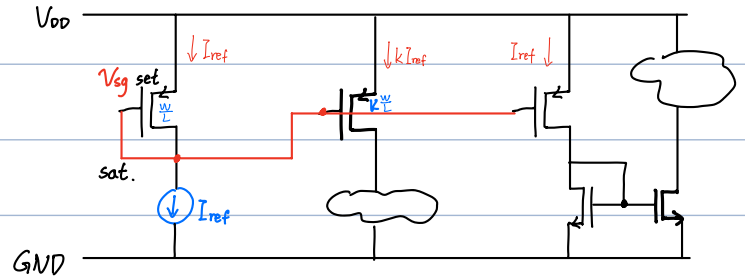

Alt ss. model (easier math)

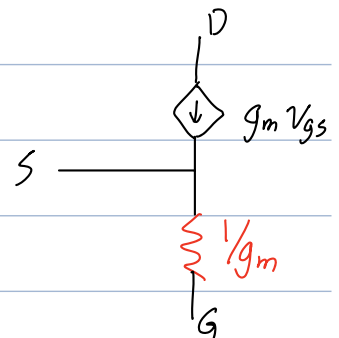$1/g_m$ cancels $\downarrow$, so i_g remains 0.



Channel width mod: non-ideal at sat.

pinchoff: $\frac{W}{L} \rightarrow \frac{W}{L-\Delta L} = \frac{W}{L} \left(\frac{1}{1+\frac{\Delta L}{L}} \right) \approx \frac{W}{L} \left(1 + \frac{\Delta L}{L} \right) \xrightarrow{\alpha} V_{DS}$

$$\tilde{I}_D = \frac{1}{2} k' \frac{W}{L} (V_{GS} - V_T)^2 \left(1 + \frac{\Delta L}{L} \right)$$




$$\approx \frac{1}{2} k' \frac{W}{L} (V_{GS} - V_T)^2 \left(1 + \lambda V_{DS} \right) \quad \frac{1}{\lambda} \equiv V_A \sim 50V \text{ (Early voltage)}$$

$$\tilde{I}_D = I_D + \frac{I_D}{V_A} V_{DS} \rightarrow \text{lin!}$$

non-ideal I source (large sig)

$$ss \quad \left. \frac{\partial i_D}{\partial V_{DS}} \right|_{\text{bias}} = \frac{I_D}{V_A} \equiv \frac{1}{r_o}$$

$r_o \sim 100k$ (want ∞)

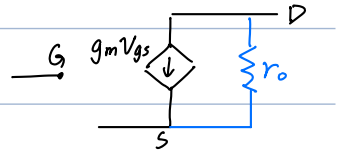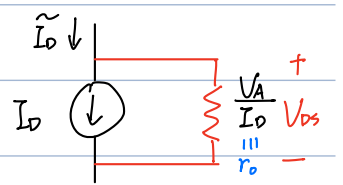
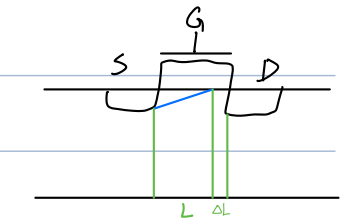


App. Current source load (more gain w/ r_o)

$V_{in,n} \rightarrow$ contradicting $\Delta i \rightarrow$ flows thru r_o (huge) $\rightarrow$ huge ΔV

$$A_v = -g_{mn} (r_{on} \parallel r_{op})$$

$$|A_v| = k'_n \frac{W}{L} V_{DD,n} \frac{V_A}{2I_D} = \frac{V_A}{V_{DD}}$$

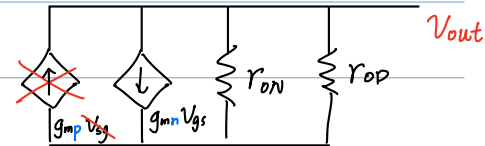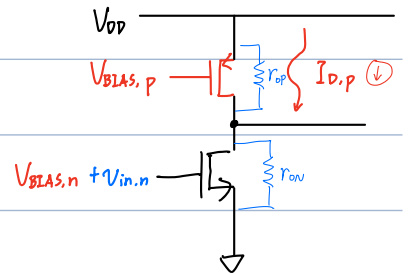

Parasitic Cap

1. gate



2. overlap

3. pn jct. cap

- Triode $C_{gs} = C_{sd} = \frac{1}{2} W L C_{ox}$

(tie S, D)


E. op amp compensation

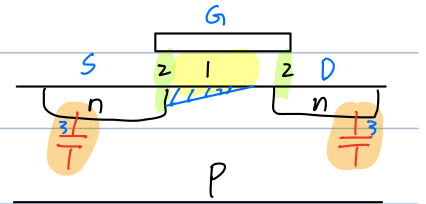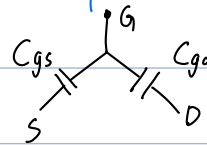

- Sat. pinched off at D side

$$C_{gs} \approx \frac{2}{3} W L C_{ox} \quad C_{gd} \text{ small, pinched}$$

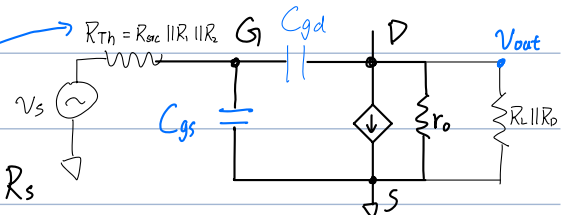High freq. Turn bias $\xrightarrow{Th} V_s = \frac{R_1 \parallel R_2}{R_{src} + R_1 \parallel R_2} V_{in} \quad R_{Th} = R_1 \parallel R_2 \parallel R_s$



Miller effect

$$i_x = j\omega C (1 + A_v) V_x \quad (\text{cap appears } 1 + A_v \text{ larger})$$

A_v can be made w/ opamp + pot $\Rightarrow$ var Cap

$$C_{gd}' \rightarrow C_{gd} (1 + g_m R_o \parallel R_L \parallel R_D) \text{ to gnd}$$

$$f_{corner} = \frac{1}{2\pi RC} = \frac{1}{2\pi R_{Th} (C_{gs} + C_{gd}' (1 + g_m (R_L \parallel R_D)))} \quad (\text{LPF})$$

$$2p/z \rightarrow 1p$$

